

[illegible]

110

Max. Marks: 20

b) A series circuit having pure resistance of $40\ \Omega$, pure inductance of 50.07mH and a capacitor connected across $400\text{V}, 50\text{Hz}$ AC supply. This R,L,C combination draws a current of 10A . Calculate i) Capacitance value ii) Power factor.