



USN

NMAM INSTITUTE OF TECHNOLOGY, NITTE*(An Autonomous Institution affiliated to VTU, Belagavi)***II Sem B.E. (Credit System) Mid Semester Examinations – II, March 2017****16EC112 – BASIC ELECTRONICS**

Duration: 1 Hour

Max. Marks: 20

*Note: Answer any One full question from each Unit.***Unit – I****Marks BT***

- a) Sketch the typical frequency response of a coupled amplifier and indicate mid frequency region, cut off frequencies and bandwidth. Why are cut off frequencies known as half power frequencies as well as 3 dB frequencies? 06 L*4
- b) A voltage amplifier having absolute voltage gain of 10 is cascaded with a power amplifier having absolute power gain of 10. Calculate the overall gain in dB. 04 L3
- a) Show the circuit of a R-C coupled oscillator using NPN transistor and explain. State the expression of oscillation. 06 L3
- b) A Hartley oscillator has $L1 = 0.2\text{mH}$ and $C = 0.2\text{ }\mu\text{H}$. Determine (i) frequency of oscillation and (ii) value of loop gain. 04 L4

Unit – II

- a) Draw circuit of OPAMP Integrator and derive expression for output voltage. Sketch the output waveform along with input waveform if input is a square wave considering time constant (RC) is a high value. 06 L4
- b) An inverting OPAMP adder has two inputs, $V1 = +2$ volts with series resistance, $R1 = 10\text{ k}\Omega$ and $V2 = -6$ volts with series resistance, $R2 = 20\text{ k}\Omega$. Feedback resistance is $40\text{ k}\Omega$ and d.c power supply is ± 9 volts. Determine output voltage for above inputs. 04 L3
4. a) Show the circuit of noninverting OPAMP amplifier and derive expression for output voltage. 05 L4
- b) With a block diagram explain operation of a communication system. 05 L3

T* Bloom's Taxonomy, L* Level

NMAM INSTITUTE OF TECHNOLOGY, NITTE

(An Autonomous Institution affiliated to VTU, Belagavi)

II Sem B.E. (Credit System) Mid Semester Examinations - I, February 2017

16EC112 – BASIC ELECTRONICS

Duration: 1 Hour

Max. Marks: 20

Note: Answer any One full question from each Unit.

Unit – I

Marks BT*

1. a) Sketch forward and reverse V-I characteristics of germanium diode. Mark cut-in voltage, dynamic resistance and reverse break-over voltage on the same and explain their significance. 6 L*2
- b) A diode bridge rectifier has an input voltage of 110 volts (rms), 60 Hz. Load Resistance is 300 ohms. Considering diodes to have conducting resistance of 5 ohms, calculate (i) average load current and (ii) % load voltage regulation. 4 L4
2. a) Draw the circuit required to obtain reverse V-I characteristic of Zener diode. Sketch the reverse V-I characteristic of Zener diode and mark the important parameters. Explain their significance. 5 L3
- b) A Zener voltage regulator has an input voltage of 24 volts and the series resistance has a value of 300 ohms. The Zener has V_Z of 12 volts. Load resistance is 1000 ohms. Obtain the value of current in Zener. If Zener has I_{ZK} of 10 mA and P_{ZM} of 500 mW, will the circuit work correctly or not and justify your answer. 5 L5

Unit – II

3. a) Draw the circuit symbols for NPN and PNP transistors. Show the current and voltage polarities for both to operate in active region. Define the parameters, common base emitter to collector current gain, α_{dc} and common emitter base to collector current gain, β_{dc} . 6 L3
- b) If an NPN transistor has β_{dc} of 200 and collector current of 50 mA, determine the values of (i) α_{dc} and (ii) base current. 4 L4
4. a) Draw circuit required to obtain input and output characteristics of NPN transistor in CB configuration. Sketch typical family of input and output characteristics. Mark regions of operation in output characteristics and explain. 6 L4
- b) If a transistor has a base current of 1 mA and β_{dc} of 100, the collector circuit DC supply of 12 volts and collector resistor of 1Kohm, (i) Calculate the value of collector current and (ii) In which region of operation is it? 4 L5

BT* Bloom's Taxonomy, L* Level

NMAM INSTITUTE OF TECHNOLOGY, NITTE

(An Autonomous Institution affiliated to VTU, Belagavi)

I Sem B.E. (Credit System) Mid Semester Examinations - I, September 2017

17EC112 – BASIC ELECTRONICS

Duration: 1 Hour

Max. Marks: 20

Note: Answer any One full question from each Unit.

Unit – I

- | | Marks | BT* |
|---|-------|-----|
| 1. a) Outline the typical forward and reverse characteristics for a silicon diode and explain the important parameters. | 6 | L*2 |
| b) A 6V Zener diode regulator circuit (with load) operates from a 10 V dc supply. It has a knee current of 5 mA and series resistance of 50 Ω . Identify the minimum value of resistance so that voltage across it does not fall below 6V. | 4 | L3 |
| 2. a) Sketch and explain the VI characteristics of the Zener diode and define its parameters V_Z , I_{ZK} , I_{ZT} and I_{ZM} . | 6 | L2 |
| b) A half-wave rectifier circuit has internal resistance of 20 Ω and load resistance of 1000 Ω from an 110V rms supply source. Calculate I_{DC} , I_{rms} and percentage load regulation. | 4 | L3 |

Unit – II

- | | | |
|---|---|----|
| 3. a) Draw the NPN transistor Common-Emitter configuration circuit and mark the regions of operation on the characteristics plot and explain the input characteristics and output characteristics. | 6 | L2 |
| b) Calculate the values of I_C , I_E and β_{dc} for a transistor with $\alpha_{dc}=0.97$ and $I_E=50\mu A$. Also, analyze the significance of transistor parameters α_{dc} and β_{dc} . | 4 | L4 |
| 4. a) Sketch the typical NPN transistor Common-Base configuration circuit and mark the regions of operation on the characteristics plot and explain the input characteristics and output characteristics. | 6 | L2 |
| b) With appropriate circuit diagrams, indicating the directions of currents and voltages, analyze the application of a transistor as an amplifier. Consider NPN transistor in the circuit. | 4 | L4 |

T* Bloom's Taxonomy, L* Level

USN

NMAM INSTITUTE OF TECHNOLOGY, NITTE*(An Autonomous Institution affiliated to VTU, Belagavi)***I Sem B.E. (Credit System) Mid Semester Examinations - II, October 2017****17EC112 – BASIC ELECTRONICS****Duration: 1 Hour****Max. Marks: 20****Note: Answer any One full question from each Unit.**

Unit – I		Marks	BT*
1.	a) Draw the frequency response of single-stage RC-coupled amplifier. Identify the significant parameters and briefly explain them.	4	L3
	b) Using suitable diagram and mathematical expressions illustrate the operation of series voltage negative feedback amplifier.	6	L2
2.	a) Calculate the frequency of oscillations of an oscillator feedback circuit with two capacitors $0.01\mu\text{F}$ and $0.001\mu\text{F}$ and an inductor $5\mu\text{H}$. Also sketch the circuit diagram of appropriate oscillator.	4	L3
	b) Outline the circuit diagram for RC phase-shift oscillator and discuss its operation.	6	L2
Unit – II			
3.	a) Draw circuit diagram for non-inverting operational amplifier (Op-amp) and develop the expression for closed loop voltage gain.	5	L3
	b) Analyse how an Op-amp can be used as an Integrator. Also derive the expression for its output voltage.	5	L4
4.	a) Using suitable circuit and equations explain the operation of an Op-amp differentiator.	5	L2
	b) Design an adder circuit using Op-amp to obtain an output voltage, $V_o = -[0.5V_1 + 0.8V_2 + 2V_3]$. Assume $R_f = 10\text{k}\Omega$.	5	L6

BT* Bloom's Taxonomy, L* Level
